

$$1. \quad Q = 300 \text{ C} \quad U = \frac{W}{Q}$$

$$\frac{W = 900 \text{ J}}{U = ?} \quad U = \frac{900 \text{ J}}{300 \text{ C}}$$

$$U = 30 \text{ V}$$

$$2. \quad U = 6 \text{ V} \quad U = \frac{W}{Q}$$

$$\frac{W = 3600 \text{ J}}{Q = ?} \quad 6 \text{ V} = \frac{3600 \text{ J}}{Q}$$

$$Q = \frac{3600 \text{ J}}{6 \text{ V}}$$

$$Q = 600 \text{ C}$$

$$3. \quad U = 220 \text{ V} \quad U = \frac{W}{Q}$$

$$\frac{Q = 3 \text{ C}}{W = ?} \quad 220 \text{ V} = \frac{W}{3 \text{ C}}$$

$$W = 220 \text{ V} \cdot 3 \text{ C}$$

$$W = 660 \text{ J}$$

$$4. \quad U = 4.5 \text{ V}$$

$$I = 0.3 \text{ A}$$

$$W = E = 0.0135 \text{ VJ} = 13.5 \text{ J}$$

$$t = ?$$

$$W = E \cdot U \cdot I \cdot t$$

$$13.5 \text{ J} = 4.5 \text{ V} \cdot 0.3 \text{ A} \cdot t$$

$$t = \frac{13.5 \text{ J}}{4.5 \text{ V} \cdot 0.3 \text{ A}}$$

$$t = 10 \text{ s}$$

$$5. \quad a \quad U = 9 \text{ V} \quad U = U_1 + U_2 + U_3$$

$$U_1 = ? \quad 9 \text{ V} = 3U_1 / 3$$

$$U_2 = ? \quad 3 \text{ V} = U_1$$

$$U_3 = ? \quad U_1 = U_2 = U_3$$

$$U_1 = 3 \text{ V}$$

$$U_2 = 3 \text{ V}$$

$$U_3 = 3 \text{ V}$$

$$b \quad U = 4.5 \text{ V} + 4.5 \text{ V} = 9 \text{ V}$$

$$U_1 = ?$$

$$U_2 = ?$$

$$U_3 = ?$$

$$U = U_1 + U_2 + U_3$$

$$9 \text{ V} = U_1$$

$$9 \text{ V} = U_2$$

$$9 \text{ V} = U_3$$

$$c \quad U = 9 \text{ V} \quad U = U_1 + U_2 \quad U = U_3$$

$$U_1 = ? \quad 9 \text{ V} = U_1 + U_2 \quad 9 \text{ V} = U_3$$

$$U_2 = ? \quad U_1 = 4.5 \text{ V}$$

$$U_3 = ? \quad U_2 = 4.5 \text{ V}$$

$$6. \quad a) \quad U_{AB} = 12 \text{ V}$$

$$b) \quad U_{AB} = 12 \text{ V} : 3 = 4 \text{ V}$$

$$c) \quad U_{AB} = 12 \text{ V}$$

A/B

1. $t = 2s$
 $Q = 4C$

$I = ?$

$I = \frac{Q}{t}$

$I = \frac{4C}{2s}$

$I = 2A$

2. $Q = 1C$
 $I = 0,04A$

$t = ?$

$t = \frac{Q}{I}$

$t = \frac{1C}{0,04A}$

$t = 25s$

3. $t = 1min = 60s$
 $I = 0,6A$

$Q = ?$

$Q = I \cdot t$

$Q = 0,6A \cdot 60s$

$Q = 36C$

4. $t_1 = 2min = 120s$
 $Q_1 = 4800C$

$I_1 = ?$

$I_1 = \frac{Q_1}{t_1}$

$I_1 = \frac{4800C}{120s}$

$I_1 = 40A$

$t_2 = 2s$

$Q_2 = 80C$

$I_2 = ?$

$I_2 = \frac{Q_2}{t_2}$

$I_2 = \frac{80C}{2s}$

$I_2 = 40A$

5. $t = 1h = 3600s$
 $I = 5A$

$Q = ?$

$Q = I \cdot t$

$Q = 5A \cdot 3600s$

$Q = 18000C$

Struje su jednake.

② (a) $I = 0,3A$

(b) $I_2 = I - I_1 = 0,5A - 0,2A = 0,3A$

(c) $I = I_1 + I_2 = 0,1A + 0,3A = 0,4A$

(d) $I_2 = I_3 = 0,3A$

② $I_1 = 0,5A$

$t = 1min = 60s$

$I_2 =$



$Q_2 = ?$

$I_2 = I : 2 = 0,5A : 2 = 0,25A$

$Q_2 = I_2 \cdot t$

$Q_2 = 0,25A \cdot 60s$

$Q_2 = 15C$

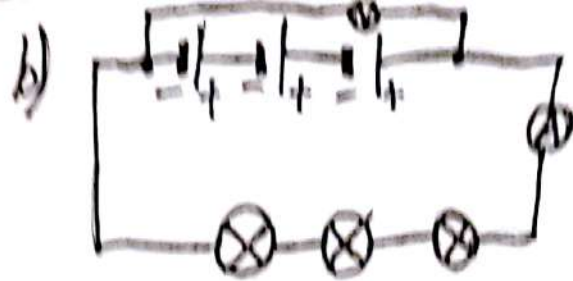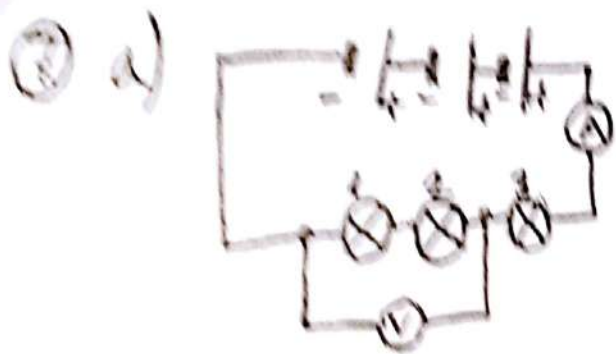

8) a) $U = 9V$

$$\frac{U_1 = 5V}{U_2 = ?}$$

$$U = U_1 + U_2$$

$$U_2 = U - U_1$$

$$U_2 = 9V - 5V$$

$$U_2 = 3V$$

$$\boxed{U_2 = 3V}$$

b) $U = 9V$

$$Q = 1C$$

$$W = ?$$

$$W = U \cdot Q$$

$$W = 9V \cdot 1C$$

$$\boxed{W = 9J}$$

c) $U_1 = 3V$

$$Q = 1C$$

$$W = ?$$

$$W = U_1 \cdot Q$$

$$W = 3V \cdot 1C$$

$$\boxed{W = 3J}$$

9) $I = 60A$

$$U = 230V$$

$$P = ?$$

$$P = U \cdot I$$

$$P = 230V \cdot 60A$$

$$\boxed{P = 13800W}$$

10) $I = 5,5A$

$$U = 220V$$

$$t = 8h = 8 \cdot 3600s = 28800s$$

$$\Delta E = W = ?$$

$$\Delta E = U \cdot I \cdot t$$

$$\Delta E = 220V \cdot 5,5A \cdot 28800s$$

$$\Delta E = 34848000J$$

$$\textcircled{11.} \quad P = 1,4 \text{ kW} = 1400 \text{ W}$$

$$\underline{t = 1 \text{ h} = 3600 \text{ s}}$$

$$W = ?$$

$$W = P \cdot t$$

$$W = 1400 \text{ W} \cdot 3600 \text{ s}$$

$$W = 5\,040\,000 \text{ J}$$

$$\textcircled{12.} \quad P = 1,2 \text{ kW} = 1200 \text{ W}$$

$$U = 220 \text{ V}$$

$$\underline{t = 4 \text{ h} = 14400 \text{ s}}$$

$$\text{a) } I = ?$$

$$P = U \cdot I$$

$$I = P : U$$

$$I = 1200 : 220$$

$$I = 5,46 \text{ A}$$

$$\text{b) } \Delta E = ?$$

$$\Delta E = P \cdot t$$

$$\Delta E = 1200 \text{ W} \cdot 14400 \text{ s}$$

$$\Delta E = 17\,280\,000 \text{ J}$$

$$\textcircled{13} \quad I = 2,5 \text{ A}$$

$$P = 275 \text{ W}$$

$$U = ?$$

$$U = P : I$$

$$U = 275 \text{ W} : 2,5 \text{ A}$$

$$U = 110 \text{ V}$$

$$\textcircled{14} \quad P = 500 \text{ W}$$

$$W = 6 \text{ kJ} = 6000 \text{ J}$$

$$t = ?$$

$$P = \frac{W}{t}$$

$$t = \frac{W}{P}$$

$$t = \frac{6000 \text{ J}}{500 \text{ W}}$$

$$t = 12 \text{ s}$$

$$\textcircled{15} \quad U = 220 \text{ V}$$

$$t = 1 \text{ h} = 3600 \text{ s}$$

$$Q = 900 \text{ C}$$

$$P = ?$$

$$I = \frac{Q}{t}$$

$$I = \frac{900 \text{ C}}{3600 \text{ s}}$$

$$I = 0,25 \text{ A}$$

$$P = U \cdot I$$

$$P = 220 \text{ V} \cdot 0,25 \text{ A}$$

$$P = 55 \text{ W}$$

$$\textcircled{16} \quad t = 14 \text{ d} = 336 \text{ h}$$

$$P = 100 \text{ W} = 0,1 \text{ kW}$$

$$\text{cijena } 1 \text{ kWh} \rightarrow 40 \text{ lp} = 0,4 \text{ kn}$$

$$\Delta E = W = P \cdot t$$

$$\Delta E = 0,1 \text{ kW} \cdot 336 \text{ h}$$

$$\Delta E = 33,6 \text{ kWh}$$

$$\text{ukupna cijena} = 33,6 \text{ kWh} \cdot 0,4 \frac{\text{kn}}{\text{kWh}}$$

$$= 13,44 \text{ kn}$$

$$\textcircled{17} \quad R = 2 \text{ k}\Omega = 2000 \Omega$$

$$U = 220 \text{ V}$$

$$I = ?$$

$$I = \frac{U}{R}$$

$$I = \frac{220 \text{ V}}{2000 \Omega}$$

$$I = 0,11 \text{ A}$$

$$\textcircled{18} \quad R = 50 \Omega$$

$$I = 0,2 \text{ A}$$

$$U = ?$$

$$U = I \cdot R$$

$$U = 0,2 \text{ A} \cdot 50 \Omega$$

$$U = 10 \text{ V}$$

(19) $R = 40 \Omega$
 $I = 25 \text{ mA} = 0.025 \text{ A}$
 $U = ?$

$$R = \frac{U}{I}$$

$$40 = \frac{U}{0.025}$$

$$U = R \cdot I$$

$$U = 40 \cdot 0.025$$

$$U = 1 \text{ V}$$

(20) $U = 220 \text{ V}$
 $R = ?$
 $I = 2 \text{ A}$

$$R = \frac{U}{I}$$

$$R = \frac{220}{2}$$

$$R = 110 \Omega$$

(21) $Q = ?$
 $R = 3 \Omega$
 $t = 2 \text{ min} = 120 \text{ s}$
 $U = 4.5 \text{ V}$

$$R = \frac{U}{I}$$

$$3 = \frac{4.5}{I}$$

$$I = 4.5 : 3$$

$$I = 1.5 \text{ A}$$

$$I = \frac{Q}{t}$$

$$1.5 = \frac{Q}{120}$$

$$Q = 1.5 \cdot 120$$

$$Q = 180 \text{ C}$$

(22) $U = 220 \text{ V}$
 $t = 3 \text{ min} = 180 \text{ s}$
 $Q = 3600 \text{ C}$
 $R = ?$

$$I = \frac{Q}{t}$$

$$I = \frac{3600}{180}$$

$$I = 20 \text{ A}$$

$$R = \frac{U}{I}$$

$$R = \frac{220}{20}$$

$$R = 11 \Omega$$

(23)

$$R_1 = 2 \Omega$$

$$R_2 = 8 \Omega$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R} = \frac{1}{2 \Omega} + \frac{1}{8 \Omega}$$

$$\frac{1}{R} = \frac{4}{8 \Omega} + \frac{1}{8 \Omega}$$

$$\frac{1}{R} = \frac{5}{8 \Omega}$$

$$R = \frac{8}{5} \Omega$$

$$R = 1.6 \Omega$$



(24) $R_1 = 7 \Omega$
 $R_2 = 5 \Omega$

$$R = ?$$


$$R = R_1 + R_2$$

$$R = 7 \Omega + 5 \Omega$$

$$R = 12 \Omega$$

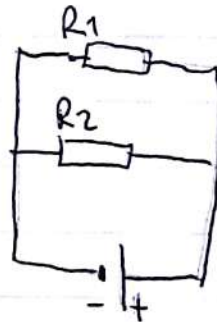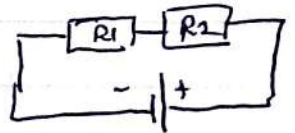

b.)

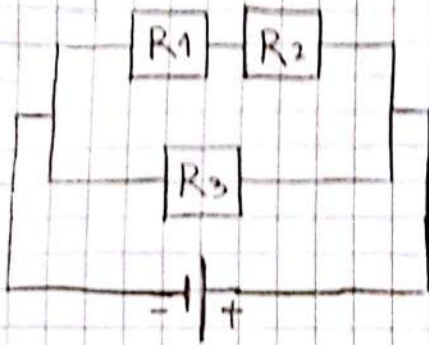

$$R_1 = 4 \Omega$$

$$R_2 = 4 \Omega$$

$$R_3 = 2 \Omega$$

$$R_5 = R_1 + R_2$$

$$R_5 = 8 \Omega$$

$$\frac{1}{R} = \frac{1}{R_5} + \frac{1}{R_3}$$

$$\frac{1}{R} = \frac{1}{8 \Omega} + \frac{1}{2 \Omega}$$

$$\frac{1}{R} = \frac{1}{8 \Omega} + \frac{4}{8 \Omega}$$

$$\frac{1}{R} = \frac{5}{8 \Omega}$$

$$R = \frac{8 \Omega}{5} \quad R = 1.6 \Omega$$

27.

a.)

$$U = 8V$$

$$I = 2A$$

Struja koja teče strujnim krugom

koji je spojen na 8V iznosi 2A

b.)

$$U = 4V$$

$$I = 1A$$

$$R = ?$$

$$I = \frac{U}{R}$$

$$R = \frac{U}{I}$$

$$R = \frac{4V}{1A}$$

$$R = 4 \Omega$$

Otpor strujnog kruga je 4Ω

c.)


$$U = 16V$$

$$I = 4A$$

Kada bi napon bio 16V

struja bi bila 4A.

28.

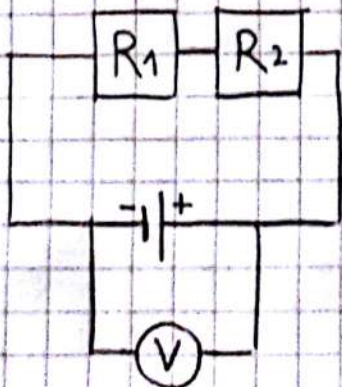

$$R_1 = 4 \Omega$$

$$R_2 = 5 \Omega$$

$$U = 4.5V$$

$$R = R_1 + R_2$$

$$R = 9 \Omega$$




$$I = ?$$

$$I = \frac{U}{R}$$

$$I = \frac{4.5V}{9 \Omega}$$

$$I = 0.5A$$

25.

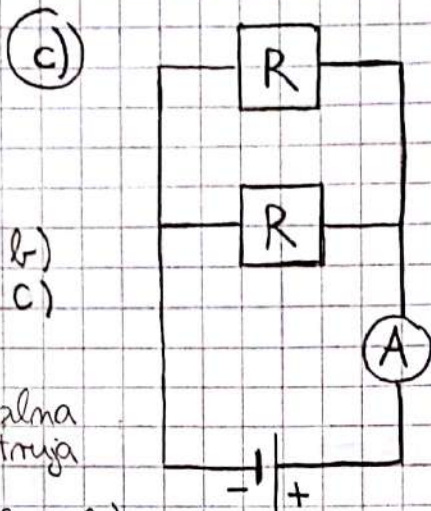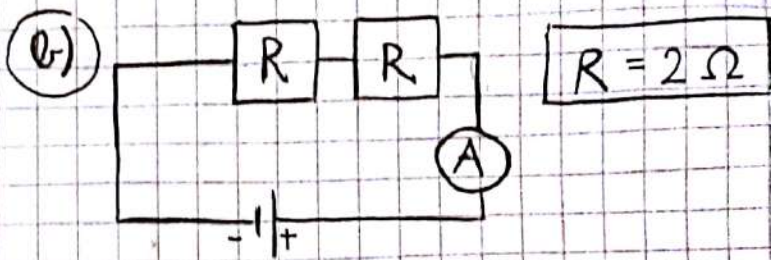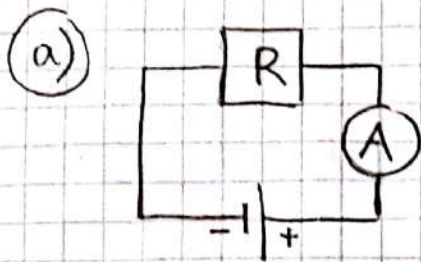

Kada bi išli

računati otpor
vidjeli bi da je
najveći na slici b)
i najmanji na c)

Pošto je struja
obrnuto proporcionalna
s otporom, najveća struja
je na slici c), a
najmanja na slici b)

a) $R = R$
 $R = 2\Omega$


b) $R = R + R$
 $R = 2\Omega + 2\Omega$
 $R = 4\Omega$

c) $\frac{1}{R} = \frac{1}{R} + \frac{1}{R}$

$\frac{1}{R} = \frac{1}{2} + \frac{1}{2}$

$\frac{1}{R} = \frac{2}{2}\Omega \quad R = 1\Omega$

26.

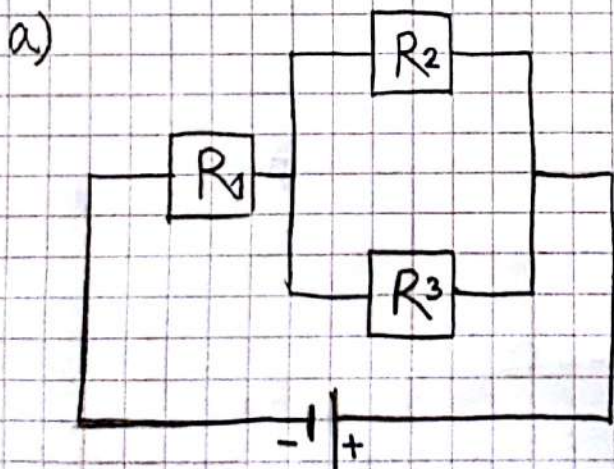

$R_1 = 4\Omega$

$R_2 = 2\Omega$

$R_3 = 2\Omega$

$R = R_p + R_1$

$R = 1\Omega + 4\Omega$

$R = 5\Omega$

$\frac{1}{R_p} = \frac{1}{R_2} + \frac{1}{R_3}$

$\frac{1}{R_p} = \frac{1}{2} + \frac{1}{2}$

$\frac{1}{R_p} = \frac{2}{2\Omega}$

$R_p = \frac{2\Omega}{2} = 1\Omega$

29

$$R_1 = 25 \Omega$$

$$R_2 = 100 \Omega$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R} = \frac{1}{25 \Omega} + \frac{1}{100 \Omega}$$

$$\frac{1}{R} = \frac{4}{100 \Omega} + \frac{1}{100 \Omega}$$

$$\frac{1}{R} = \frac{5}{100 \Omega}$$

$$R = 20 \Omega$$


$$U = 220V$$

$$I = ? \quad I = \frac{U}{R}$$

$$I = \frac{220V}{20 \Omega}$$

$$I = 11 A$$

30

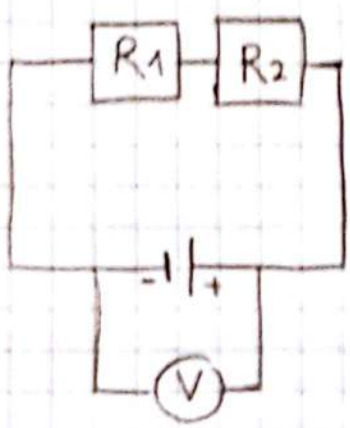

$$R_1 = 6 \Omega$$

$$R_2 = 4 \Omega$$

$$U = 20V$$

$$a) R = R_1 + R_2$$

$$R = 6 \Omega + 4 \Omega$$

$$R = 10 \Omega$$

- Usporni otpor je 10 Ω

b)

$$R = 10 \Omega$$

$$I = \frac{U}{R}$$

$$U = 20V$$


$$I = \frac{20V}{10 \Omega}$$

$$I = ?$$

$$I = 2A$$

- Krugom teče struja od 2A

c)

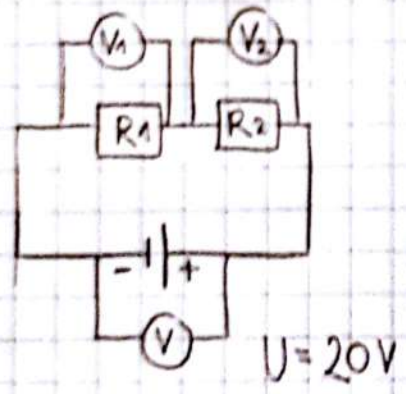

$$U_1 = ?$$

$$U_2 = ?$$

$$U_2 = U - U_1$$

$$I = 2A$$

$$U_1 = I \cdot R_1$$

$$U_2 = 20V - 12V$$

$$R_1 = 6 \Omega$$

$$U_1 = 2A \cdot 6 \Omega$$

$$U_2 = 8V$$

$$R_2 = 4 \Omega$$

$$U_1 = 12V$$